



# Applied Electronics I

**Mock Model Exam Questions  
with their detailed Answers**

1. When the temperature of a doped semiconductor increased, its Conductivity\_\_

A) Increases or Decreases depending on whether it is P –or N-type

B) Decreases

C) Does not change

D) Increases

- Answer: D) ✓ When the temperature of a doped semiconductor is increased, the number of charge carriers increases since the thermal energy supplied to electrons in the valence band forces them to excite to the conduction band. As a result, the number of electrons in conduction band increases and holes in valence band increases so, conductivity increases.

2. In N type semiconductor, the position of Fermi level:


A) In Conduction Band

B) Near Conduction Band

C) Near Valance Band

D) In Valance Band

Answer: B) Near Conduction Band ✓

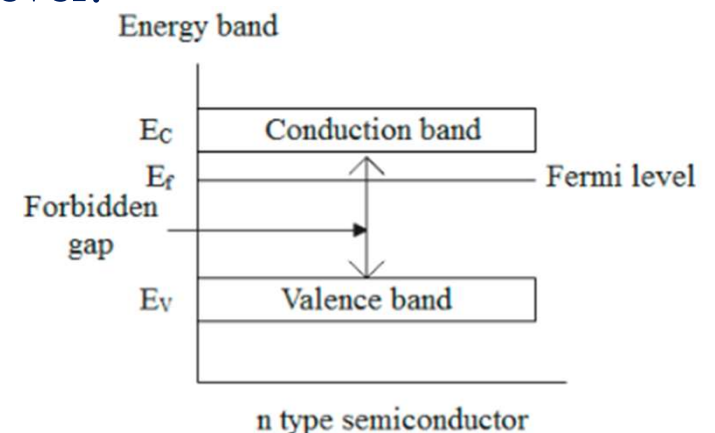

3. When the crystal diode current is large, the bias is\_\_\_\_\_

- A) Forward
- B) Small
- C) Large
- D) Reverse

Answer: A) ✓

4. You have an application for a diode to be used in a tuning circuit. A type of diode to use might be;

- A) Schottky diode
- B) Gunn diode
- C) An LED diode
- D) Varactor diode

Answer: D) ✓

**Varactor diode** is a simple variable capacitor that allows oscillator and other circuits to be easily tuned by applying a voltage

**5.** The forward characteristic of a diode has a slope of approximately 20mA/V at a desired point. The approximate incremental resistance of the diode is:

- A)  $50\Omega$
- B)  $20\Omega$
- C)  $35\Omega$
- D)  $10\Omega$

- Answer: A) ✓ The reciprocal of the slope of I-V graph gives the resistance of diode as:  $1/\text{slope} = 1/(20 \times 10^{-3} \text{ A/V}) = 50\Omega$

**6.** The process of emitting photons from a semi-conductive material is called\_\_\_\_\_

- A) Gallium Phosphide
- B) Electroluminescence
- C) Gallium Arsenide
- D) Photoluminescence

- Answer: **B)** ✓ **Electroluminescence** is a process by which photons are generated when the excess electron–hole pairs are created by an electric current caused by an externally applied bias

7. In a PNP transistor, the current carriers are\_\_\_\_\_

- A) Holes
- B) Acceptor Ions
- C) Free Electrons
- D) Donor Ions

Answer: A) ✓ In a pnp transistor, current carriers are holes b/c holes are existed in excess amount than free electrons.

8. What configuration is widely preferred in cascading amplifier?

- A) Common Source
- B) Common Emitter
- C) Common Collector
- D) Common Base

- Answer: B) ✓ **Common Emitter configuration** offers both current and voltage gain resulting in higher power gain than the other configurations

**9.** The lowest output Impedance is obtained in case of BJT amplifiers for:

- A) CE with RE Configuration
- B) CC Configuration
- C) CE Configuration
- D) CB Configuration

- Answer: B) ✓ The **CC amplifier configuration** has the lowest output Impedance compared to the other BJT Configurations

**10.** When transistors are used in digital circuits, they usually operate in the\_\_\_\_\_

- A) Saturation and Cutoff Region
- B) Breakdown Region
- C) Linear Region
- D) Active Region

Answer: A) ✓ Since digital circuit is an electrical circuit that uses binary logic to process binary data either (0 or 1). Zero refers OFF while 1 represent ON.

A Transistor is used in digital circuits as ON switch in Saturation mode and OFF switch in Cutoff Mode

**11.** Often a common collector will be the last stage before the load.

The main function of this stage is:

- A) To buffer the voltage amplifiers from the low resistance load and provide impedance matching for maximum power transfer
- B) To provide phase inversion of the input signal
- C) Provide a high frequency path to improve the frequency response
- D) To provide voltage gain at the load

Answer: A) ✓

**12.** An N channel D-MOSFET with a positive VGS is operating in\_\_\_\_\_

- A) The Depletion mode
- B) Cutoff mode
- C) The Enhancement mode
- D) Saturation mode

Answer: C) ✓ The operating region with positive VGS in N channel D-MOSFET is called Enhancement operational region

**13.** Enhancement mode MOSFETs are more commonly used as

- A) Buffers
- B) Resistors
- C) Switches
- D) Capacitors

Answer: C) ✓



**14.** The total gain of a multistage amplifier is less than the product of the gains of individual stages due to\_\_\_\_\_

- A) Loading effect of the next stage
- B) Power loss
- C) The use of many transistors
- D) The use of many capacitors

Answer: A) ✓

**15.** What happens to the bandwidth if the total gain increased in cascade amplifiers?

- A) Increases
- B) Infinite
- C) Remains the same
- D) Decreases

Answer: D) ✓ In cascade amplifiers voltage gain increases which in turn reduces the bandwidth to maintain a constant gain-bandwidth product.

**16.** If  $A_v$ ,  $A_i$  and  $A_p$  represents the voltage gain, current gain and power gain ratio of an amplifier which of the following is correct expression for the corresponding values in decibel?

A) Current gain:  $10\log(A_v)$  dB

B) Power gain:  $20\log(A_p)$  dB

C) Power gain:  $10\log(A_p)$  dB

D) Voltage gain:  $10\log(A_v)$  dB

Answer: C) ✓

**Since**

Current gain:  $20\log(A_i)$  dB

Voltage gain:  $20\log(A_v)$  dB

Power gain:  $10\log(A_p)$  dB


**17.** The main characteristics of a Darlington Amplifier are:

- A) High input Impedance, Low output Impedance and High Current gain
- B) High input Impedance, High output Impedance and High Current gain
- C) Low input Impedance, Low output Impedance and High Current gain
- D) Low input Impedance, Low output Impedance and Low Current gain

Answer: A) ✓

**Darlington Amplifier** has

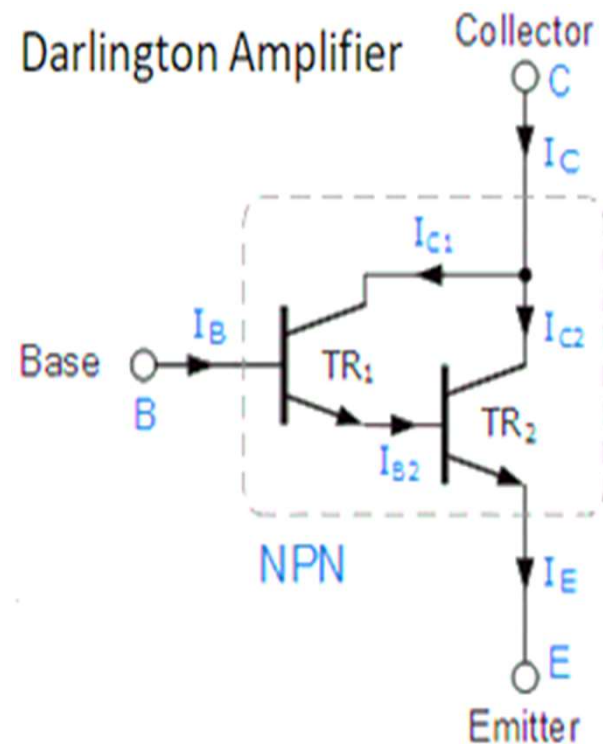- High input Impedance,
- Low output Impedance
- High Current gain



**Good Luck**