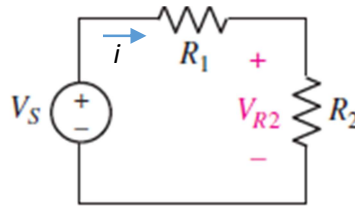


1. A new type of device appears to accumulate charge according to the expression $q(t) = (15t^2 - 12t) \text{ mC}$ (t in s) in the interval of $0 \leq t < 5 \text{ s}$, at what time does the current flowing into the device equal zero?

A. 0.8s
B. 0.4s
C. 0.475s
D. 0.2ms

Answer: B


2. Which of the following is not true regarding to the following circuit shown below.



A. $V_s = i(R_1 + R_2)$
B. $V_{R2} = V_s \left(\frac{R_2}{R_1 + R_2} \right)$
C. $V_{R2} = V_s \left(\frac{R_1}{R_1 + R_2} \right)$
D. $i = \left(\frac{V_s}{R_1 + R_2} \right)$

Answer: C

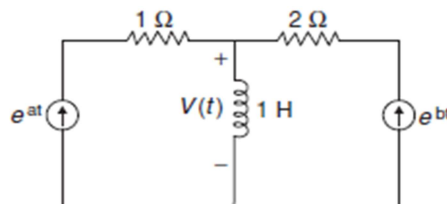
3. In the circuit given below, the voltage $V(t)$ is given by



A. $e^{at} - e^{bt}$
B. $e^{at} + e^{bt}$
C. $a.e^{at} - b.e^{bt}$
D. $a.e^{at} + b.e^{bt}$

Answer: D

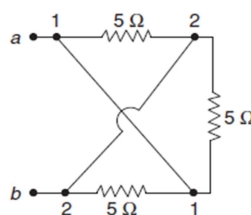
4. Consider the circuit shown in figure below and determine R_{ab} ,



A. 2.5Ω
B. 7.5Ω
C. 25Ω
D. 1.66Ω

Answer: D

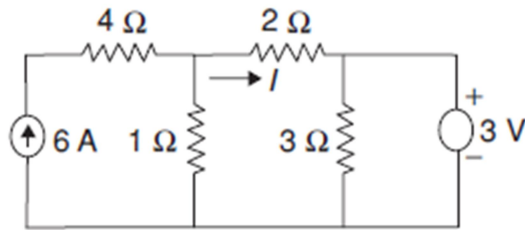
5. For the circuit shown in the figure the current 'I' is given by



- A. 2 A
- B. 3 A
- C. 1 A
- D. zero

Answer: C

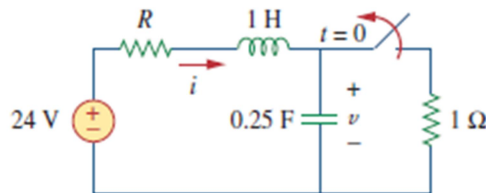
6. The switch in the circuit below is closed for long time and opened at $t = 0$. What is the value of v (capacitor voltage) at steady state?



- A. 1V
- B. 24V
- C. 0V
- D. 6V

Answer: B

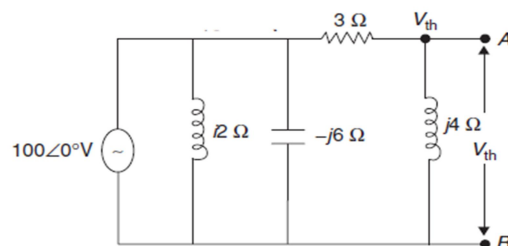
7. The Thevenin's equivalent voltage V_{th} across the terminal A and B of the network shown in the figure is given by



- A. $(64+48j)V$
- B. $(48j - 64)V$
- C. $(48 + 64j)V$
- D. $(48 - 64j)V$

Answer: A

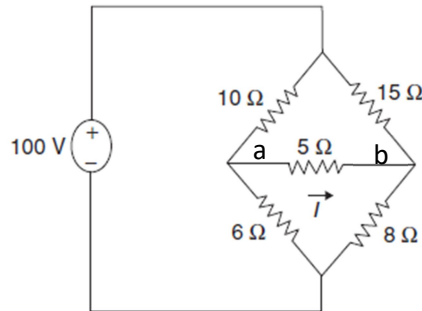
8. What is the Thevenin equivalent resistance at terminal **a** and **b** on 5Ω indicated on the circuit given below



- A. 9.44Ω
- B. 39Ω
- C. 8.97Ω
- D. 9Ω

Answer: C

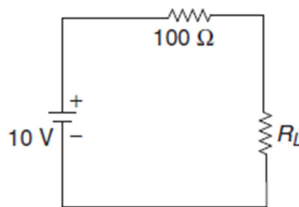9. The maximum power that can be transferred to the load resistor R_L from the voltage source in the figure is



- A. 1 W
- B. 10 W
- C. 0.25 W
- D. 0.5 W

Answer: C

10. What happens if the following program is executed in C and C++?

```
#include<stdio.h>
int main(void)
{
    int new = 5;
    printf("%d", new);
}
```

- A. Error in C and successful execution in C++
- B. Error in both C and C++
- C. Error in C++ and successful execution in C
- D. A successful run in both C and C++

Answer C

11. Which of the following is the correct identifier?

- A. \$var_name
- B. VAR_123
- C. varname@
- D. 2come

Answer B

12. Which of the following statements is correct about the formal parameters in C++?
- A. Parameters with which functions are called
 - B. Parameters which are used in the definition of the function
 - C. Variables other than passed parameters in a function
 - D. Variables that are never used in the function

Answer A

13. What will be the output of the following C++ code?

```
#include <stdio.h>
#include <iostream>
using namespace std;
int main()
{
    int array[] = {10, 20, 30};
    cout << -2[array];
    return 0;
}
```

- A. -15
- B. -30
- C. compile time error
- D. garbage value

Answer B

14. What will be the output of the following C++ code?

```
#include <iostream>
using namespace std;
int main()
{
    int a = 3, b = 4;
    cout << a | b;
    return 0;
}
```

- A. 3
- B. 4
- C. 7
- D. 8

Answer C

15. For inserting a new line in C++ program, which one of the following statements can be used?

- A. \n
- B. \r
- C. \a
- D. \t

Answer A

16. Which of the following gives the 4th element of the array?

- A. Array;
- B. array[0];
- C. array[3];
- D. array[4];

Answer C

17. What is the output of below program?

```
int main()
{
    int a = 10;
    cout<<a++;
    return 0;
}
```

- A. 10
- B. 11
- C. 12
- D. 9

Answer A

18. A zener diode is always connected in

- A. Reverse bias
- B. Forward bias
- C. either reverse or forward bias
- D. none of the above

Answer: A

19. Which type of rectifier required transformer to operate

- A. half-wave rectifier
- B. center-tap full-wave rectifier
- C. bridge full-wave rectifier
- D. none of the above

Answer: B

20. A Bipolar junction transistor is acted as

- A. Current controlled device
- B. voltage controlled device
- C. both voltage and current operated device
- D. none of the above

Answer: A

21. A transistor is connected in CB mode. If it is not connected in CE mode with same bias voltages, the values of base, collector and emitter current will

- A. remain the same
- B. increase
- C. decrease
- D. none of the above

Answer: A

22. Main function of common-collector stage is to

- A. provide voltage gain
- B. provide phase inversion
- C. provide a high-frequency path to improve the frequency response
- D. buffer the voltage amplifiers from the low-resistance load and provide impedance matching for maximum power transfer

Answer: D

23. A silicon transistor is biased with base resistor method. If values of $\beta=100$, $V_{BE}=0.7$ V, zero signal collector current $I_C = 1$ mA and $V_{CC} = 6$ V , what is the value of the base resistor ?

- A. 105 k Ω
- B. 530 k Ω
- C. 315 k Ω
- D. None of the above

Answer: B

24. The purpose of capacitors in a transistor amplifier is to

- A. Protect the transistor
- B. Cool the transistor
- C. Couple or bypass a.c. component
- D. Provide biasing

Answer: C

25. The best frequency response of amplifier is achieved using

- A. RC coupling
- B. Transformer coupling
- C. Direct coupling
- D. None of the above

Answer: C

26. Why the number of stages that can be directly coupled is limited

- A. Due to changes in temperature cause thermal instability
- B. Circuit becomes heavy and costly
- C. It becomes difficult to bias the circuit
- D. None of the above

Answer : A

27. The period of signal of $x(t) = \sin t + \cos \sqrt{2}t$ is

- A. $\pi/\sqrt{2}$
- B. 3π
- C. 2π
- D. The signal is not periodic

Answer: D

28. The even part of a signal $x(n) = u(n) + u(-n)$ is

- A. $u(n) - u(-n)$
- B. $u(n) + u(-n)$
- C. $u(-n) - u(n)$
- D. $2u(n)$

Answer: B

29. The Impulse response of a LTI system is given as $h(n) = \left(\frac{-1}{4}\right)^n u(n)$. The step response is

- A. $\frac{1}{4} \left[5 + \left(\frac{-1}{4}\right)^n \right]$
- B. $\frac{1}{4} \left[5 - \left(\frac{-1}{4}\right)^n \right]$
- C. $\frac{1}{4} \left[4 + \left(\frac{-1}{4}\right)^n \right]$
- D. $\frac{1}{4} \left[4 - \left(\frac{-1}{4}\right)^n \right]$

Answer: B

30. $H(s)$ the transfer function and $H(s) = \frac{s}{s^2 - s - 2}$ ($\sigma < -1$). Then the function is

- A. Causal and stable
- B. Causal and unstable
- C. Non-causal and stable
- D. Non-causal and unstable


Answer: D

31. Unit impulse response of a system is $f(t) = e^{-t}$, for $t \geq 0$, for this system, the steady state value of the output for unit step input is equal to

- A. 1
- B. -1
- C. 0
- D. ∞

Answer: A

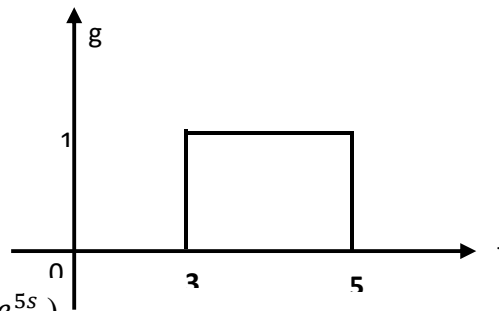32. The Laplace transform of the following signal given in the following figure is equal to:



- A. $\frac{1}{s}(e^{3s} - e^{5s})$
- B. $\frac{1}{s}(e^{-5s} - e^{-3s})$
- C. $\frac{1}{s}(e^{3s} - e^{5s})$
- D. $\frac{e^{-3s}}{s}(e^{5s} - e^{3s})$

Answer: D

33. $x[n] = a^n u[n]$ where a is real. z-transform of $x[n]$ is

- A. $\frac{z}{z-a}$, $|z| < |a|$
- B. $\frac{z}{z-a}$, $|z| > |a|$
- C. $\frac{z}{z+a}$, $|z| > |a|$
- D. $\frac{z}{z+a}$, $|z| < |a|$

Answer: B

34. Which of the following statements is/are true?

1. A Fourier series for an even periodic function will consist entirely of cosine terms.
2. A Fourier series for an odd periodic function will consist entirely of sine terms.
3. A Fourier series for an odd periodic function will consist entirely of cosine terms.
4. A Fourier series for an even periodic function will consist entirely of sine terms.

- A. 3, 4
- B. 1, 2
- C. 1, 3
- D. 2, 4

Answer: B

35. If the driving point admittance function of a 1-port network is $Y(s) = \frac{Ks}{s+\alpha}$, it can be realized using

- A. Parallel combination of R, L
- B. Series combination of R, L
- C. Parallel combination of R, C
- D. Series combination of R, C

Answer D

36. For an RC driving point impedance function, the poles and zeros

- A. Should alternate only on the negative real axis
- B. Should alternate on the imaginary axis
- C. Should alternate on real axis
- D. Can lie anywhere on the left half plane

Answer A

37. An ideal filter should have

- A. Zero attenuation in the attenuation band
- B. Zero attenuation in the pass band
- C. Infinite attenuation in the passband
- D. None of the above

Answer B

38. If two two-port networks are connected in parallel, and if the port current requirement is satisfied, which one of the following is true

- A. The ABCD-parameter matrices add
- B. The z-parameter matrices add
- C. The y-parameter matrices add
- D. None of the above

Answer C

39. Match the List-I (Forms) with List-II (Networks)

	List I		List II
a	Cauer I	1	L in series arms and C in shunt arms of a ladder
b	Cauer II	2	C in series arms and L in shunt arms of a ladder
c	Foster I	3	series combination of L and C in parallel
d	Foster II	4	Parallel combination of L and C in series

- A. a-1, b-2, c-3, d-4
- B. a-1, b-2, c-4, d-3
- C. a-2, b-1, c-4, d-3
- D. a-2, b-1, c-3, d-4

Answer A

40. A two-port network is described by relations

$$V_1 = 2V_2 + 0.5I_2$$

$$I_1 = 2V_2 + I_2$$

What is the value of the h_{22} parameter of the network

- A. $2\ \Omega$
- B. 2 mho
- C. -2Ω
- D. -2 mho

Answer D

41. Ideal response of filter takes place in

- A. Pass band and stop band frequency
- B. Stop band frequency
- C. Pass band frequency
- D. None of the mentioned

Answer C

42. A network function can be completely specified by

- A. Poles and zeros
- B. Real parts of zeros
- C. Real parts of poles
- D. Poles, zeros, and a scale factor

Answer D

43. A device that is used to switch one of several input lines to a single output line is called a

- A. Comparator
- B. Multiplexer
- C. Decoder
- D. Encoder

Answer C

44. If the period of a clock signal is 500 ps, the frequency is _____

- A. 20 MHz
- B. 2 GHz
- C. 200 MHz
- D. 20 GHz

Answer B

45. In the binary number 1000, the weight of the column with the 1 is

- A. 8
- B. 10
- C. 6
- D. 4

Answer A

46. 2's complement of binary number 0101 is

- A. 1111
- B. 1011
- C. 1101
- D. 1110

Answer B

47. _____ is a universal gate

- A. AND
- B. OR
- C. NOT
- D. NAND

Answer D


48. A Boolean expression that is in standard SOP/POS form is

- A. The minimum logic expression
- B. Contains only one product term
- C. Has every variable in the domain in every term
- D. None of the above

Answer C

49. Assume Q_0 is LOW. The next clock pulse will cause

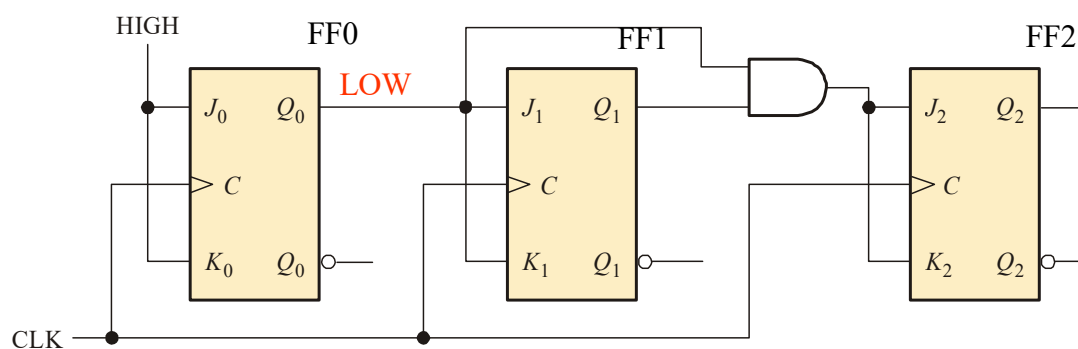- a. FF1 and FF2 to both toggle
- b. FF1 and FF2 to both latch
- c. FF1 to latch; FF2 to toggle
- d. FF1 to toggle; FF2 to latch



Answer B

50. A 4-bit parallel-in/parallel-out shift register will store data for

- A. 1 clock period
- B. 3 clock periods
- C. 2 clock periods
- D. clock period

Answer A

51. The chemical used in breather for transformer should have the quality of

- A. cooling the transformer oil
- B. cleansing the transformer oil
- C. absorbing moisture
- D. ionizing air

Answer C

52. Power factor of a synchronous motor is unity when

- A. the armature current is maximum
- B. the armature current is zero
- C. the armature current is maximum
- D. none of the above

Answer C

53. A synchronous motor can operation at

- A. lagging, leading and unity power factors
- B. unity power factor only
- C. leading power factor only
- D. lagging power factor only

Answer A

54. No load on a transformer is carried out to determine

- A. efficiency of the transformer
- B. magnetizing current
- C. copper loss
- D. magnetizing current and loss

Answer D

55. In a D.C. shunt motor, under the conditions of maximum power, the current in the armature will be

- A. more than full load current
- B. less than full load current
- C. rated full load current
- D. almost negligible

Answer A

56. A 4pole Lap wound DC shunt generator has an armature winding consists of 220 turns each of 0.004Ω . The armature resistance is..

- A. 0.5Ω
- B. 1Ω
- C. 0.025Ω
- D. 0.055Ω

Answer D

57. Which of the following motors has the poorest speed regulation?

- A. cumulative compound motor
- B. differential compound motor
- C. series motor
- D. hunt motor


Answer C

58. In D.C. generator, lap winding is used for

- A. low voltage, low current
- B. high voltage, low current
- C. low voltage, high current
- D. high voltage, high current

Answer C

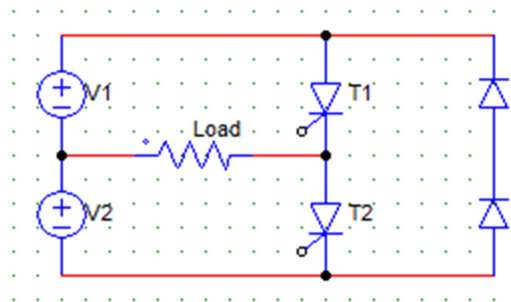59. What is the voltage across the R load when only T2 is conducting?



- A. V_s
- B. $V_s/2$
- C. $2V_s$
- D. Zero

Answer B

60. The output current wave of a single-phase full bridge inverter on RL load is

- A. a sine wave
- B. a square wave
- C. a triangular wave
- D. constant dc


Answer C

61. In AC voltage controllers the

- A. variable ac with fixed frequency is obtained
- B. variable ac with variable frequency is obtained
- C. variable dc with fixed frequency is obtained
- D. variable dc with variable frequency is obtained

Answer A

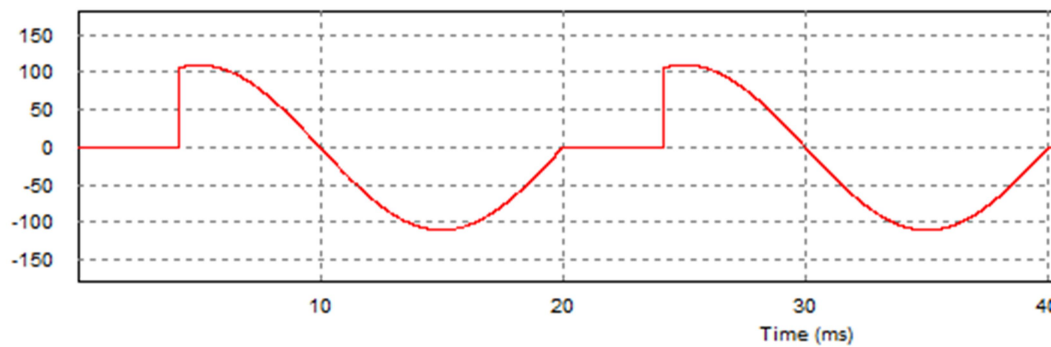62. The below given output voltage waveform can be obtained by a



- A. half wave ac voltage controller
- B. full wave ac voltage controller
- C. half wave controller with firing angle = 0° for T1
- D. full wave controller with firing angle = 0° for both T1 and T2

Answer B

63. A cycloconverter is a _____

- A. one stage power converter
- B. one stage voltage converter
- C. one stage frequency converter
- D. none of the mentioned

Answer C

64. Induction heating is a _____ type of heating

- A. zero frequency
- B. high frequency
- C. power frequency
- D. none of the mentioned

Answer B

65. Servo motors are an example of which type of load?

- A. Pulsating loads
- B. Short time loads
- C. Impact loads
- D. Short time intermittent loads

Answer B

66. The peak inverse voltage in ac to dc converter system is highest in

- A. single phase full converter
- B. single phase full wave midpoint converter
- C. 3 phase half wave converter
- D. 3 phase bridge converter

Answer B

67. Earthing is necessary to give protection against

- A. Electric shock
- B. Voltage fluctuation
- C. Overloading
- D. High temperature of the conductors

Answer A

68. The fuse rating is usually defined in

- A. Ampere
- B. Kilowatt
- C. VA
- D. All of the above

Answer A

69. Fuse wire should be connected to

- A. Phase wire only
- B. Neutral wire only
- C. Ground wire only
- D. Both B and C

Answer A

70. If 2 switches are connected in series to a lamp/load, then

- A. Any one switch needs to be switched ON to energize the load
- B. Both the switches need to be switched ON to energize the load
- C. Only switch 1 need to be switched ON to energize the load
- D. Only switch 2 need to be switched ON to energize the load

Answer B

71. The connection sequence of meter and circuit breaker is

- A. circuit breaker must be connected before meter
- B. meter must be connected before circuit breaker
- C. A and B
- D. none

Answer B

72. the rate of circuit breaker for general purpose branch circuit is

- A. 16ampere
- B. 10ampere
- C. 25ampere
- D. a and b

Answer D

73. The architect design is approved by

- A. Client
- B. Tender
- C. Contractor
- D. all

Answer A

74. The standard distance between two socket is

- A. 1.21 meter
- B. 0.61 meter
- C. 1.83 meter
- D. None

Answer C

75. what is the difference between agreement and contract

- A. contract is only legally enforceable
- B. an agreement must be socially acceptable
- C. an agreement doesn't be enforceable by the law
- D. all

Answer D

76. Bundled conductors in EHV transmission lines

- A. decrease inductance
- B. decrease capacitance
- C. increase inductance
- D. increase capacitance

Answer A

77. Which of the following insulator is practically used for railway crossings?

- A. string insulator
- B. strain insulator
- C. pin insulator
- D. all of the above

Answer B

78. Communication lines are treated as

- A. medium transmission lines
- B. long transmission lines
- C. short transmission lines
- D. any of the above


Answer B

79. The horizontally placed conductors of a single-phase line operating at 50 Hz are having outside diameter of 1.6 cm, and the spacing between centers of the conductors is 6 m. The permittivity of free space is 8.854×10^{-12} F/m. The capacitance to ground per kilometer of each line is

- A. 4.2×10^{-9} F
- B. 8.4×10^{-9} F
- C. 4.2×10^{-12} F
- D. 8.4×10^{-12} F

Answer B

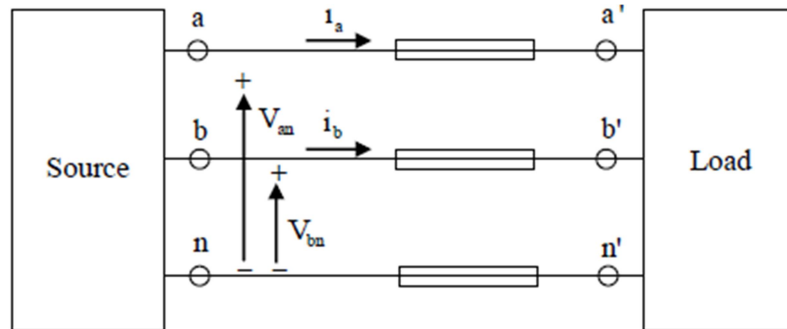80. A source is supplying a load through a 2-phase, 3-wire transmission system as shown in figure below. The instantaneous voltage and current in phase-a are $V_{an} = 220\sin(100\pi t)$ V and $i_a = 10\sin(100\pi t)$ A, respectively. Similarly for phase-b the instantaneous voltage and current are $V_{bn} = 220\cos(100\pi t)$ V and $i_b = 10\cos(100\pi t)$ A, respectively.



- A. 2200W
- B. $2200\sin^2(100\pi t)$ W
- C. 440
- D. $2200\sin(100\pi t)\cos(100\pi t)$ W

Answer A


81. Transmission lines are transposed to reduce
- A. interference with neighboring communication lines
 - B. proximity effect
 - C. skin effect
 - D. ferranite effect

Answer A

82. Transmission loss is
- A. a function of bus voltage magnitude and its angle
 - B. a function of reactive power generation
 - C. independent of real power generation
 - D. a function of real power generation

Answer D

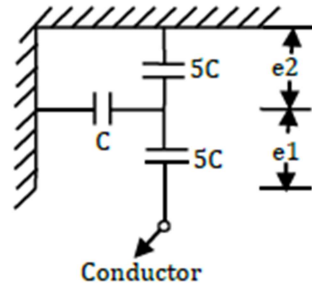83. Consider a three-phase, 50Hz, 11kV distribution system. Each of the conductors is suspended by an insulator string having two identical porcelain insulators. The self-capacitance of the insulator is 5 times the shunt capacitance between the link and the ground, as shown in the figure. The voltage across the two insulators are



- A. $e_1 = 3.74 \text{ kV}$, $e_2 = 2.61 \text{ kV}$
- B. $e_1 = 3.46 \text{ kV}$, $e_2 = 2.89 \text{ kV}$
- C. $e_1 = 6.0 \text{ kV}$, $e_2 = 4.23 \text{ kV}$
- D. $e_1 = 5.5 \text{ kV}$, $e_2 = 5.5 \text{ kV}$

Answer B

84. The insulation resistance of the 20km long underground cable is $8\text{M}\Omega$. Other things being same, the insulation resistance of 10km long cable will be

- A. $8\text{M}\Omega$
- B. $4\text{M}\Omega$
- C. $16\text{M}\Omega$
- D. $32\text{M}\Omega$

Answer C

85. In case of short circuit, _____ current will flow in the circuit

- A. Zero
- B. Very low
- C. Normal
- D. Very high current

Answer D

86. The service mains connects

- A. Distributor and consumer terminals
- B. Distributor and transformer
- C. Distributor and relay system
- D. Transformer and earth

Answer A

87. A type of relay works on the principle of either electromagnetic induction or electromagnetic attraction is

- A. Electromagnetic relay
- B. Static relay
- C. Numerical relay
- D. None

Answer A

88. Power Frequency Variations are usually caused by rapid changes in

- A. Customer
- B. Load
- C. a and b
- D. all

Answer D

89. Expected failure rate is the inverse of

- A. Expected repair rate
- B. Mean time to failure
- C. Mean time repair
- D. b and c

Answer B

90. _____ is a mechanism for interchange of power between two and more utilities which provide of generate electricity.

- A. Power Pool
- B. Automatic voltage control
- C. Load frequency control
- D. None

Answer A

91. Over current protection is

- A. None directional
- B. No intentional time delay
- C. Relay responds to overcurrent condition in the forward direction only
- D. a and b

Answer D

92. _____ relay is a gas operated relay used for the protection of oil immersed transformers against all the types of internal faults

- A. Static relay
- B. Numerical relay
- C. Buchholz Relay
- D. Electromechanical relay

Answer C

93. Most nuclear reactors are controlled by means of control rods that are made of _____

- A. Boron
- B. Cadmium
- C. Hafnium
- D. All of the above

Answer D

94. Which sentence is not correct

- A. Microgrid can be considered as a small-scale version of the traditional utility grid
- B. Microgrid can coordinate unique community energy needs with generation resources
- C. Microgrid have to operate with utility grid
- D. Microgrid enables 'intelligent sharing' of energy loads and resources

Answer C

95. The main types of sources in Microgrid are

- A. Only renewables
- B. Renewables, diesel generators, microturbine, fuel cell
- C. Only diesel generators
- D. Renewables and diesel generators

Answer B

96. The thermodynamic Isochoric process shows constant _____ process

- A. Enthalpy
- B. Pressure
- C. Volume
- D. Temperature

Answer C

97. _____ cycle is the example for external combustion thermodynamic power cycle

- A. Ericsson
- B. Otto
- C. Diesel
- D. Brayton

Answer A

98. It is a measure of the ignition quality of diesel engine fuels

- A. Octane number
- B. Cetane number
- C. Pour point
- D. None of the above

Answer B

99. Which of the following are types of systems used in ocean thermal energy conversion?

- A. Horizontal and vertical
- B. Vertical and open cycle
- C. Open cycle and closed cycle
- D. Horizontal and closed cycle

Answer C

100. Open cycle ocean thermal energy conversion systems use _____ as the working fluid.

- A. Vapour from rivers
- B. Water from rivers
- C. Vapour from seawater
- D. Seawater

Answer C